

Name: Beverly Abadines (004737953) and Kyle Lee (005054981)

Class: CSE 401

Term: Spring 2016

Lab 2: The MIPS datapath in Verilog: the Instruction Decode stage

Introduction: This lab implements the second stage of the MIPS five stage pipeline. This stage consists of four components: control, register, s_extend, and id_ex.

control:

Receives 6 bits of the instruction code from ifetch.v (originally 32 bits) as an opcode and divides it into execution/address, memory access, and write-back control lines. This module applies switch statements and should be used for review.

register:

The module populates thirty-two 32-bit addresses/registers with zero. For lab 2, RegWrite data is unspecified, but eventually it should come from MEM/WB from lab 6. This outputs two 32-bit registers,

A and B. A is the contents of register rs (source) and B is the contents of registers rt (target).

s_extend:

Sign extends 16 bits into 32 bits. This maintains the characteristics of a positive or negative number.


id_ex:

Implements an ID/EX pipeline register that inputs and outputs the program counter and instruction.

Changes from the diagram: ctlex_out outputs into regdst[1], alusrc[1], and aluop[2]

This refers to the Execution/Address control lines.

Timing Diagram for register

 


Name: Beverly Abadines (004737953) and Kyle Lee (005054981)

Class: CSE 401

Term: Spring 2016

Timing Diagram for s_extend

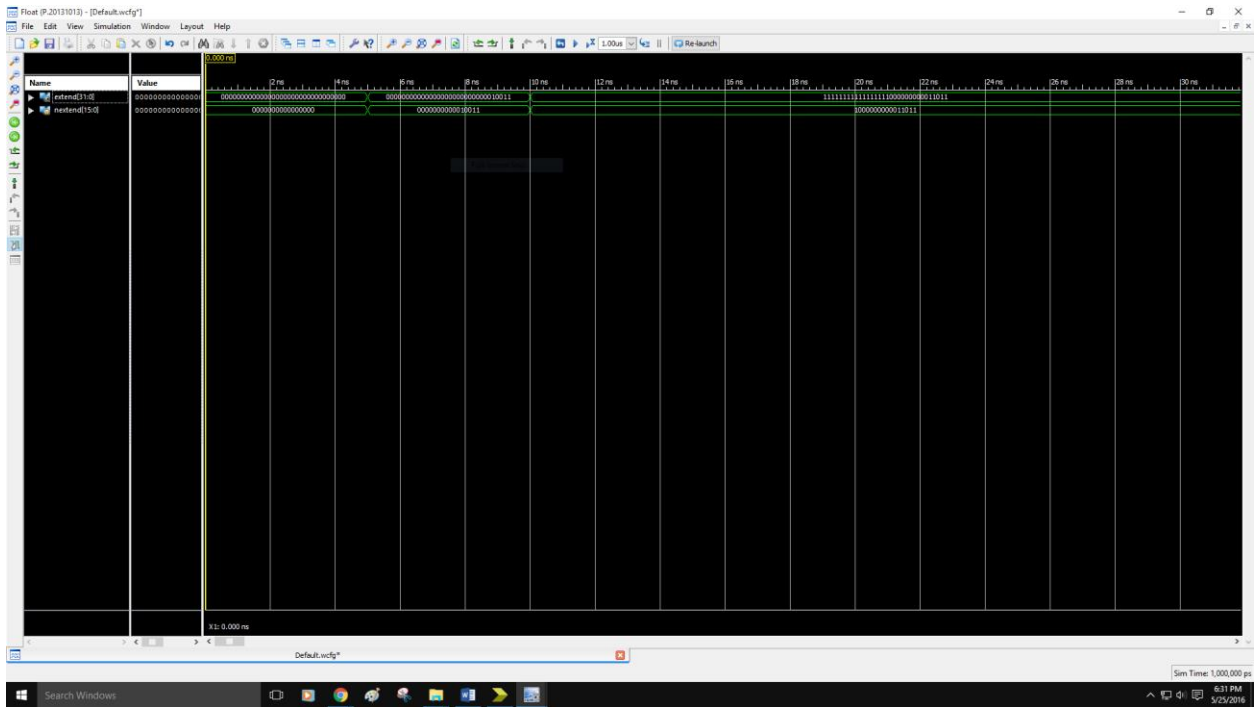

Timing Diagram for Pipeline ID Stage

